



**United International University**  
*QUEST FOR EXCELLENCE*

DEPT. ELECTRICAL AND ELECTRONIC ENGINEERING

ELECTRICAL WIRING AND DRAFTING [EEE 2200]

TRIMESTER - SPRING 241

SECTION – A

**PROJECT SPECIFICATION:** Designing a 3451+ sq ft of 5 storied building [located at 416no. house, word 14, Narayanganj, Bangladesh] with civil layout, fitting fixture layout, conduit layout, SB calculation, SB group calculation, SB grouping, SB connection diagram, SDB calculation, SDB connection diagram. And designing the full building with MDB calculation, MDB connection diagram, single line diagram, lightning protection setup, earthing system, light calculation, PV system, rooftop PV connection setup, fire detection and protection system layout.

PRESENTED BY  
Joyanta Debnath  
ID: 021182032

PRESENTED TO  
S M Monzurul Haque Chowdhury  
Lecturer, Dept. of EEE

---


## PROJECT INDEX

- ✓ Civil Layout
- ✓ Fitting & Fixture Layout
- ✓ Conduit Layout
- ✓ Light Loads Connection
- ✓ Heavy Loads Connection
- ✓ Switch Board & SDB Connection
- ✓ Junction & MDB Connection
- ✓ Switch Board Calculation
- ✓ Switch Board Connection & Groups
- ✓ SDB & MDB Calculation
- ✓ Sub-Distribution Board Diagram
- ✓ Main-Distribution Board Diagram
- ✓ Load Division
- ✓ Single Line Diagram for Substation
- ✓ PV Calculation
- ✓ PV Diagram
- ✓ Earthing System
- ✓ Lightening Protection System
- ✓ Emergency Fire Protection System

[3451+ sq ft of 5 storied building]

NOTE: ALL LAYOUT, DESIGN, SYMBOL, CALCULATION etc. are done according to BNBC 2020


CIVIL LAYOUT

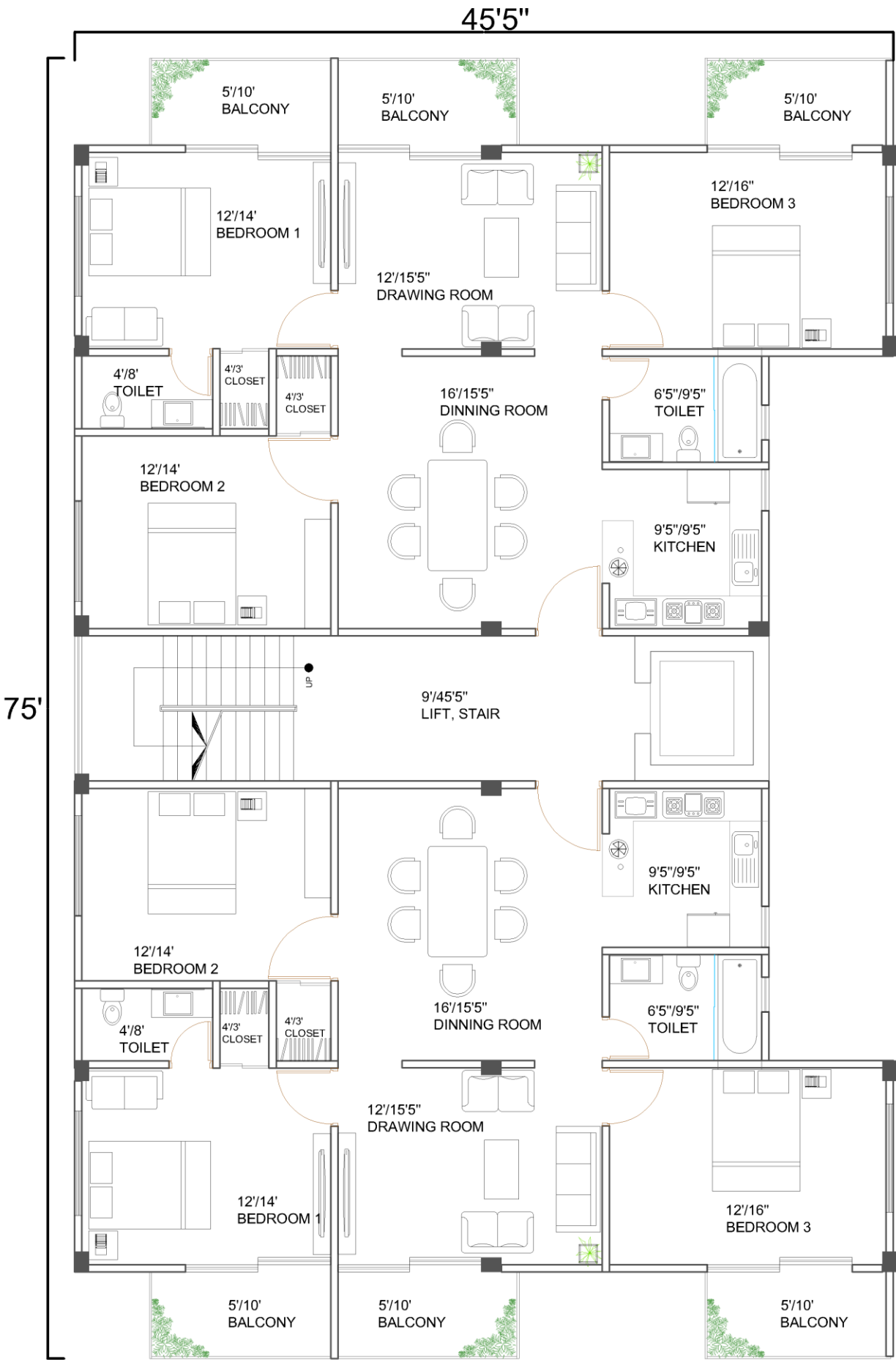

3412 SQFT, 5 STORIED BUILDING



LEGEND

LAYOUT 1

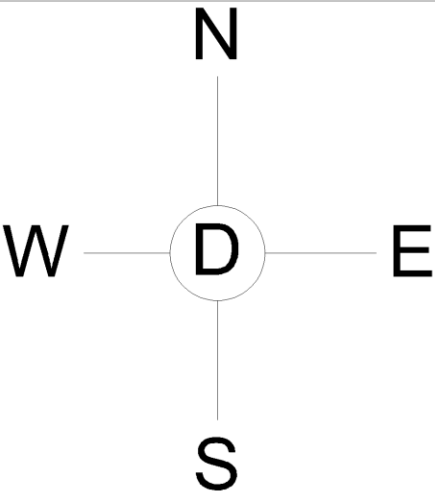

Faculty Name:  
S M Monzurul Haque Chowdhury  
Drawing Title: Civil layout  
Scale: Inch & Foot  
Student Name: Joyanta Debnath  
ID: 021182032

# FITTINGS AND FIXTURES LAYOUT

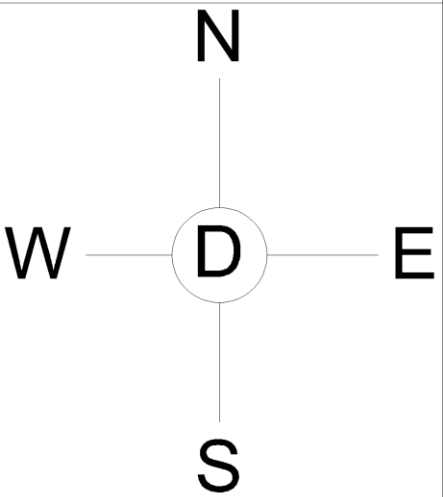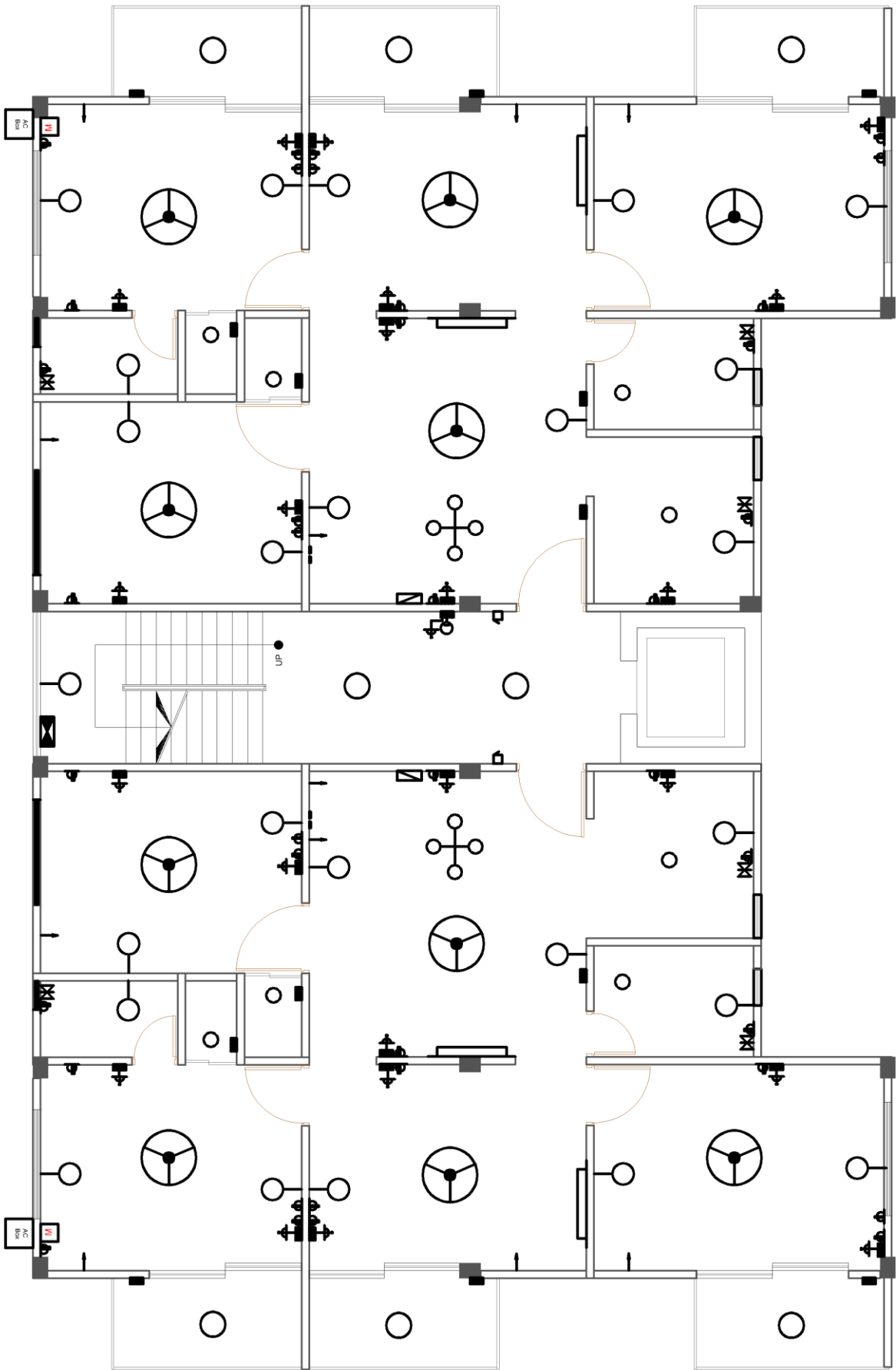

Symbol	Descriptive Name
○	Ceiling light
⦿	Lintel level lamp
▬	Fluorescent wall light
⊗	Ceiling fan
⬢	Calling bell
▲	3pin 15amp socket
△	2pin 5amp socket
■	Exhaust fan
▣	AC
▤	AC box
▪	Switch board
▬	SDB
■	MDB
⋮	Antenna junction box
⋮	Telephone junction box
-	Telephone grommet
⊕	4point chandelier light
•	Push button
▲	2pin TV socket


Faculty Name:  
S M Monzurul Haque Chowdhury

Drawing Title: Civil layout

Scale: Inch & Foot


Student Name: Joyanta Debnath  
ID: 021182032

# CONDUIT LAYOUT

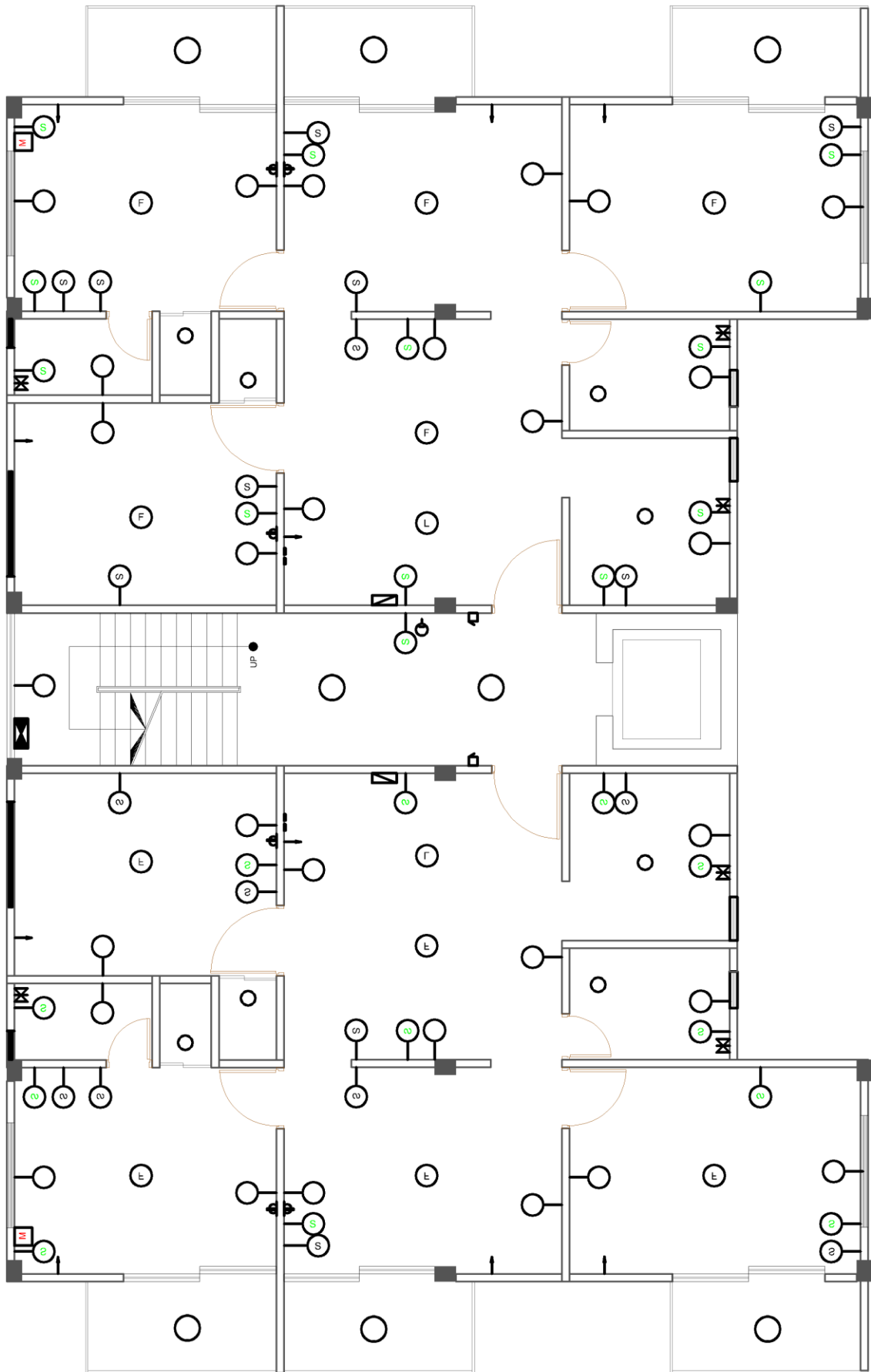

## LEGEND

### LAYOUT 1

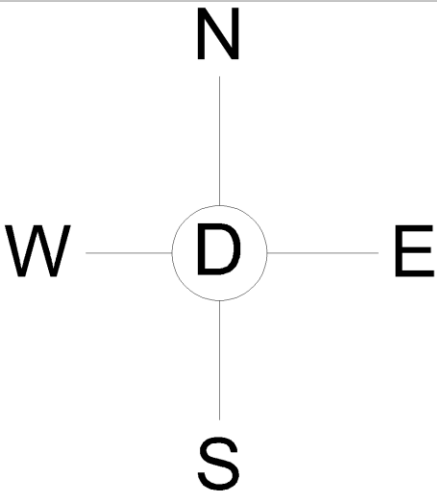

Symbol	Descriptive Name
	Lintel level light
	Fluresent wall light
	3pin 15amp socket
	2pin 5amp socket
	3pin 15amp socket at lintel level
	3pin 5amp socket at SB
	Ceiling fan
	Ceiling bell
	K - Type light
	Exhaust
	2pin T V antenna Socket
	AC
	4 point Chandelier
	Push button
	Telephone grommet
	Switch board
	SDB
	MDB
	Antenna junction box
	Telephone junction box
	Mirror light


Faculty Name:  
S M Monzurul Haque Chowdhury

Drawing Title: Civil layout

Scale: Inch & Foot


Student Name: Joyanta Debnath  
ID: 021182032

# CONDUIT LAYOUT FOR LIGHT LOAD

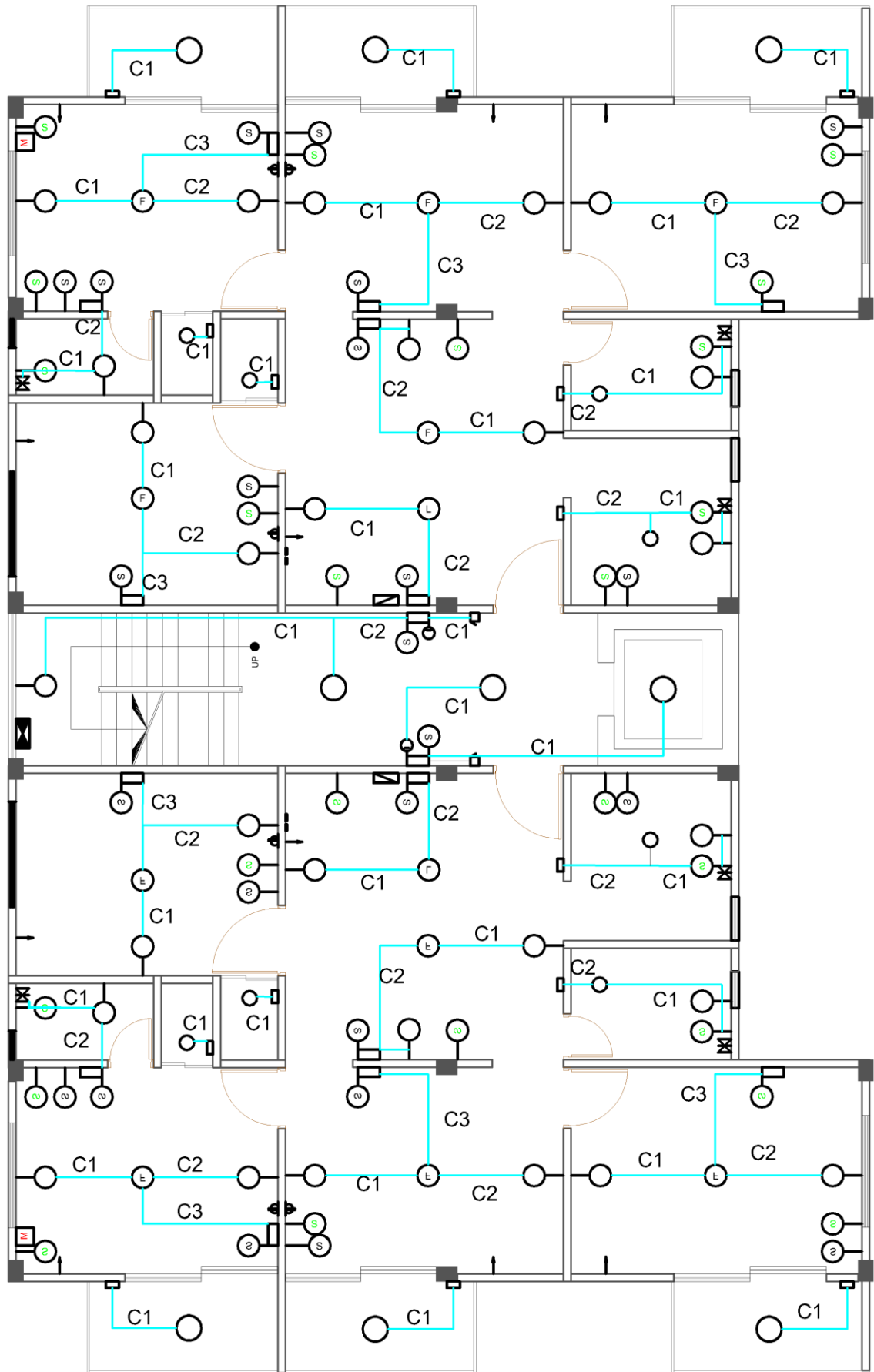

## LEGEND

### LAYOUT 1

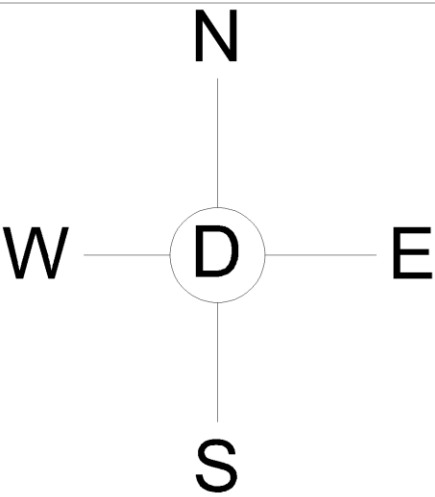

C1 - 2\*1.5mm<sup>2</sup>

C2 - 4\*1.5mm<sup>2</sup>

C3 - 6\*1.5mm<sup>2</sup>

C5 - 2\*4mm<sup>2</sup>

C6 - 2\*6mm<sup>2</sup>


C22 > 2 \* C2 > 8\*1.5 2

C1,22 - C1 + C22

Faculty Name:  
S M Monzurul Haque Chowdhury  
Drawing Title: Civil layout


Student Name: Joyanta Debnath  
ID: 021182032

# CONDUIT LAYOUT FOR HEAVY LOAD

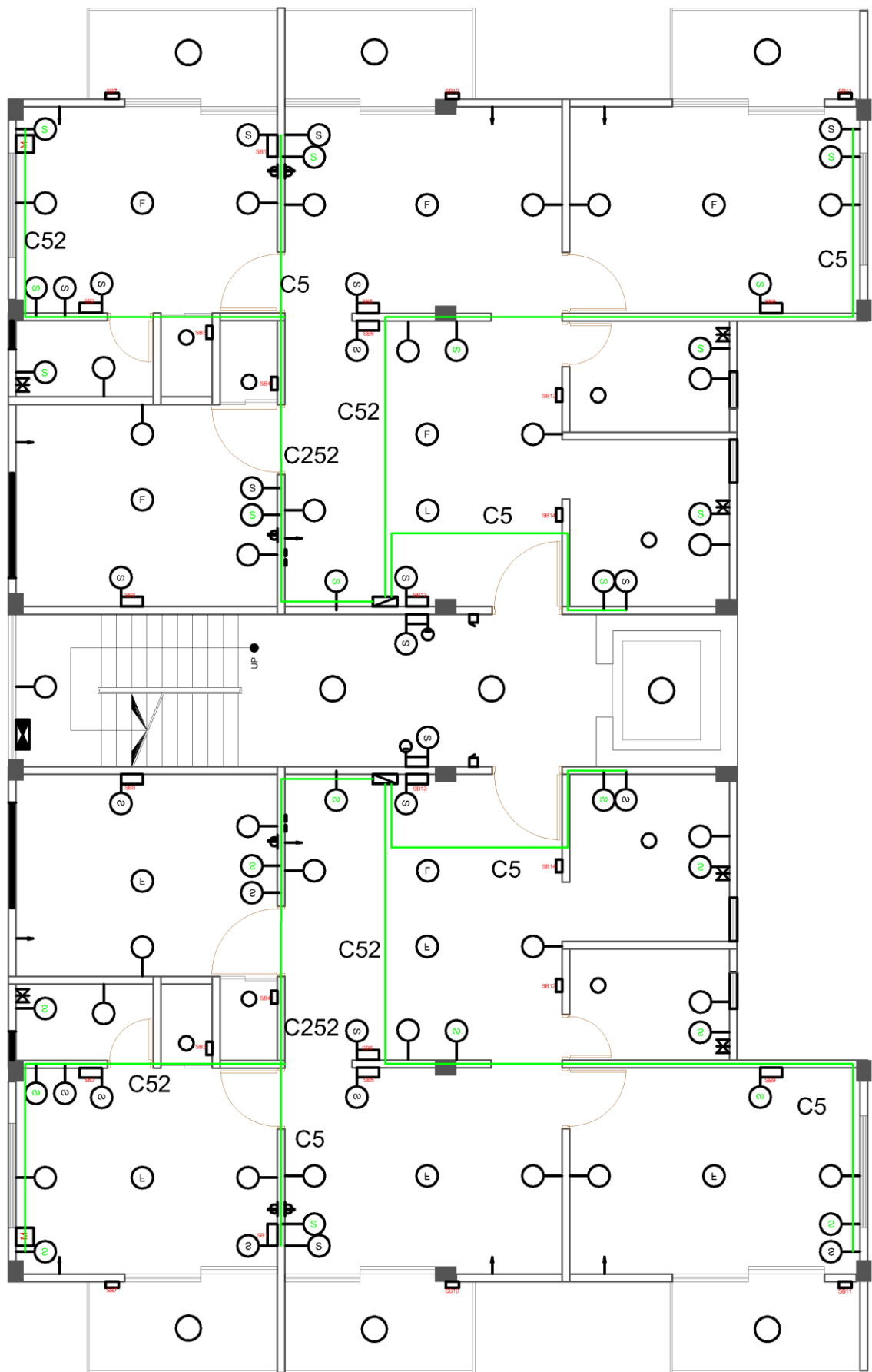

## LEGEND

### LAYOUT 1

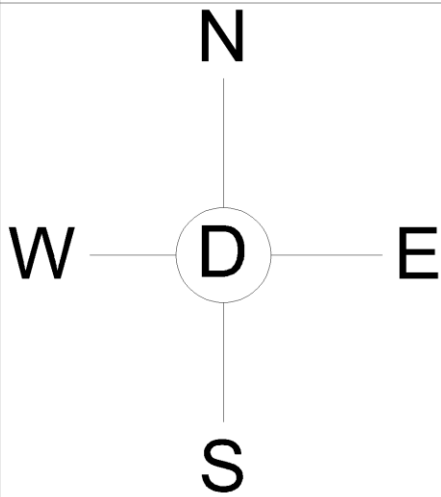

C5 - 2\*4mm<sup>2</sup>

C52 - 4\*4mm<sup>2</sup>

C5,52 = C5 + C52  
=2\*4mm<sup>2</sup> + 4\*4mm<sup>2</sup>

C52,252=C52+2\*C52

C6 - 2\*6mm<sup>2</sup>


C26 - 2\*C6,2c

C6,C26=C6+C26,3

Faculty Name:  
S M Monzurul Haque Chowdhury  
Drawing Title: Civil layout


Student Name: Joyanta Debnath  
ID: 021182032
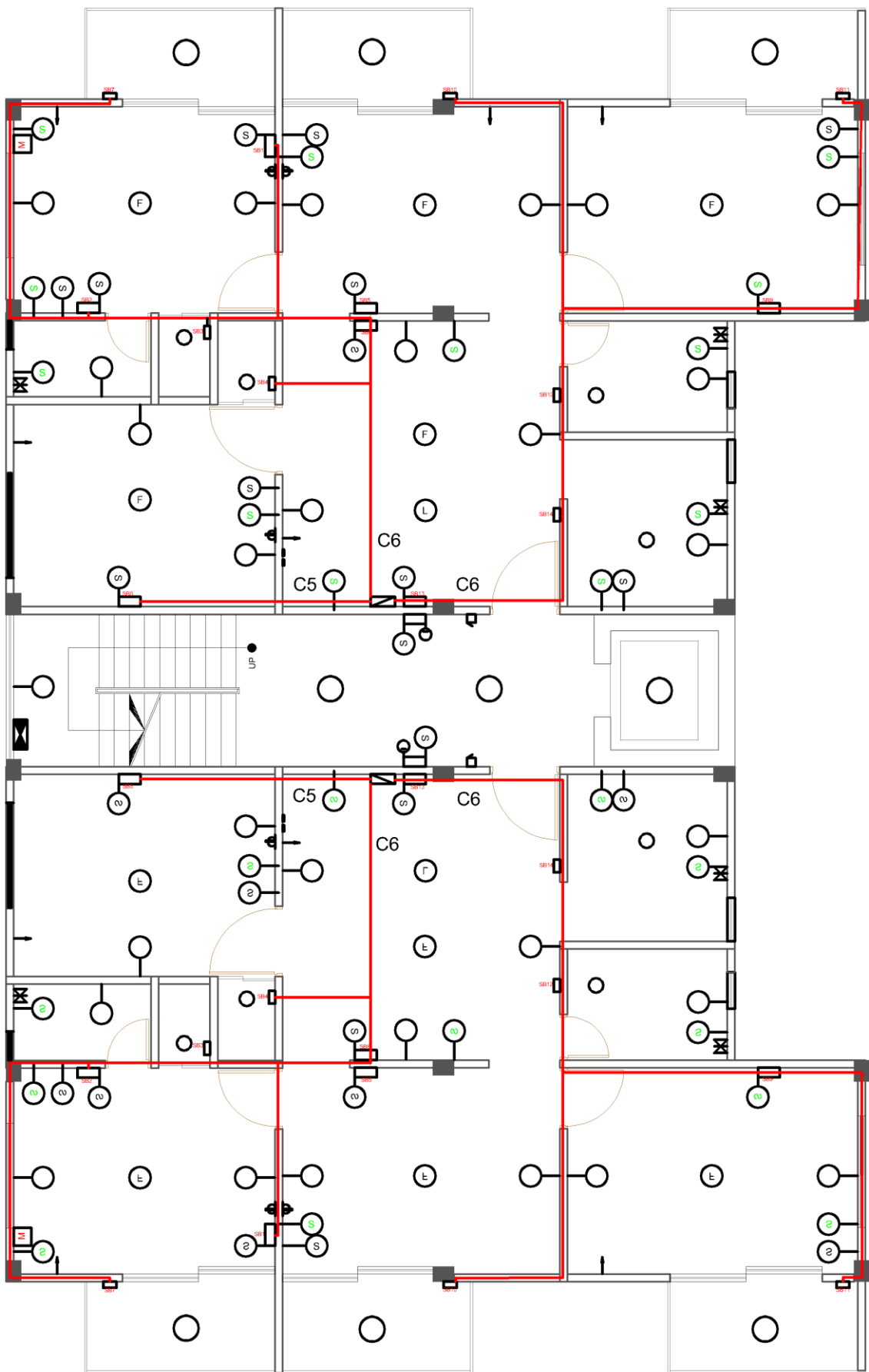
# CONDUIT LAYOUT FOR SWITCHBOARD GROUPING AND CONNECTION



## LEGEND

### LAYOUT 1

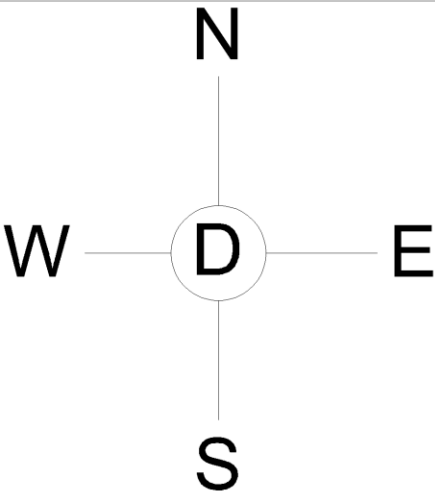

C5 - 2\*4mm<sup>2</sup>

C52 - 4\*4mm<sup>2</sup>

C5,52 = C5 + C52  
= 2\*4mm<sup>2</sup> + 4\*4mm<sup>2</sup>

C52,252=C52+2\*C52

C6 - 2\*6mm<sup>2</sup>

C26 - 2\*C6,2c


C6,C26=C6+C26,3

Faculty Name:  
S M Monzurul Haque Chowdhury  
Drawing Title: Civil layout

Student Name: Joyanta Debnath  
ID: 021182032



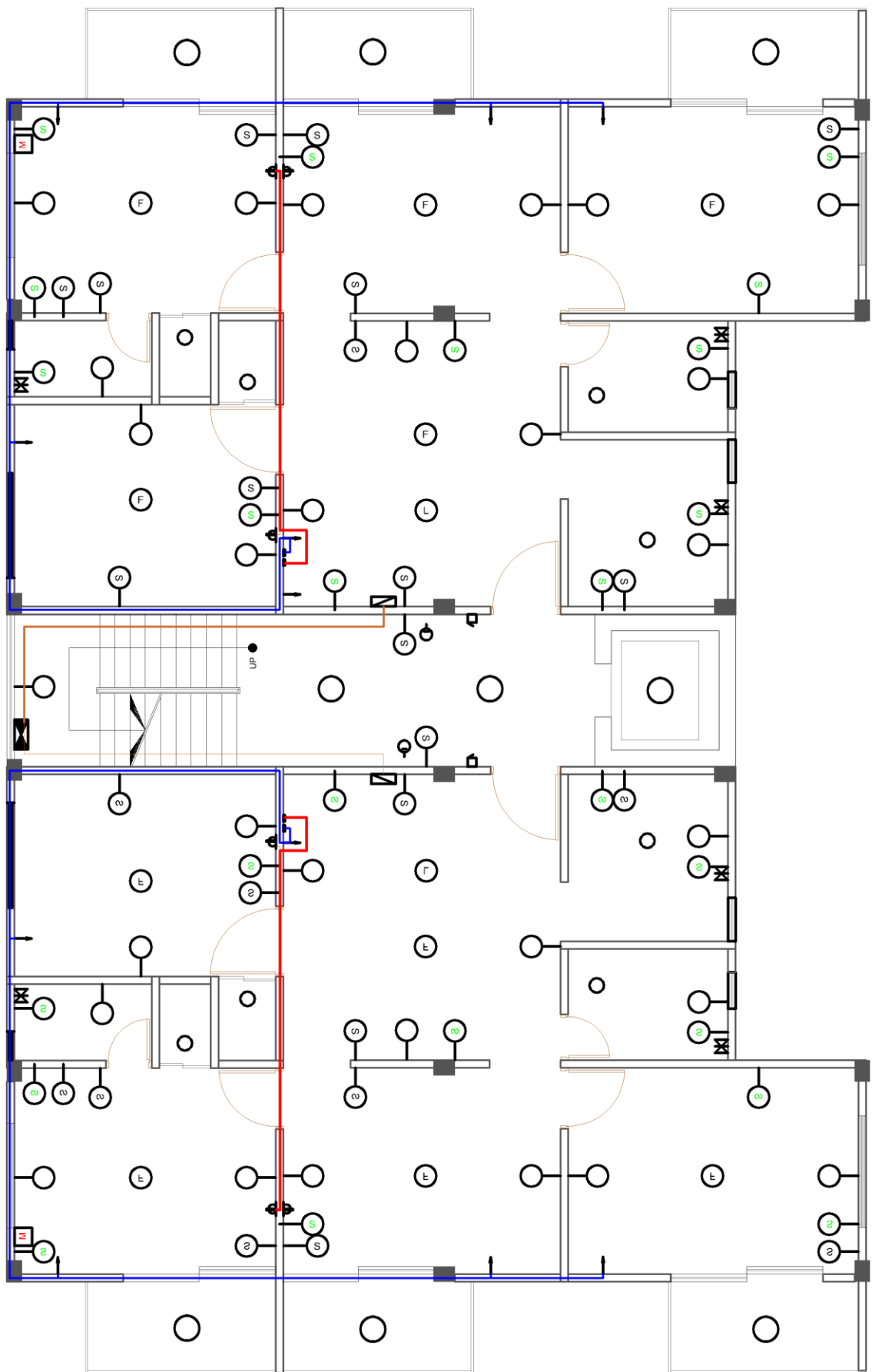
# CONDUIT LAYOUT FOR ANTENNA JUNCTIONS AND MDB CONNECTION



## LEGEND

### LAYOUT 1

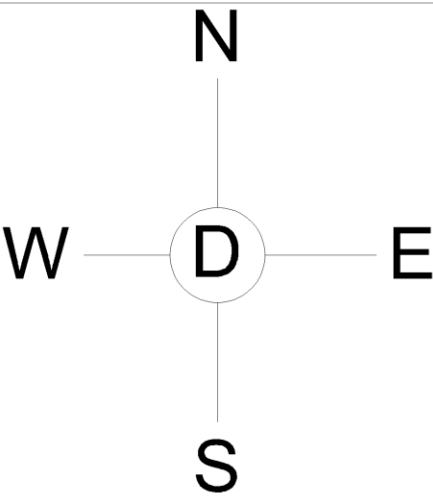

C5 - 2\*4mm<sup>2</sup>

C52 - 4\*4mm<sup>2</sup>

$$C5,52 = C5 + C52 \\ = 2*4mm^2 + 4*4mm^2$$

$$C52,252 = C52 + 2*C52$$

C6 - 2\*6mm<sup>2</sup>

C26 - 2\*C6,2c

$$C6,C26 = C6 + C26,3$$

Faculty Name:  
S M Monzurul Haque Chowdhury  
Drawing Title: Civil layout

Student Name: Joyanta Debnath  
ID: 021182032

# CALCULATION FOR SWITCHBOARD

## Switchboard-1

- Light= 2\*40W
- Fan= 1\*80W
- TV Socket= 1\*500W
- 2pin Socket= 1\*500W

Total= 1160W  
 $P = V * I * 0.9$   
Here,  
 $I = 1160 / 230 * 0.9 = 5.6A$

## Switchboard-2

- Light= 1\*40W
- Exhaust Fan= 1\*60W
- 2pin Socket= 1\*500W

Total= 600W  
 $P = V * I * 0.9$   
Here,  
 $I = 600 / 230 * 0.9 = 2.9A$

## Switchboard-3

- Light= 1\*18W

Total= 18W  
 $P = V * I * 0.9$   
Here,  
 $I = 18 / 230 * 0.9 = 0.09A$

## Switchboard-4

- Light= 1\*18W

Total= 18W  
 $P = V * I * 0.9$   
Here,  
 $I = 18 / 230 * 0.9 = 0.09A$

## Switchboard-5

- Light= 2\*40W
- Fan= 1\*80W
- TV Socket= 1\*500W
- 2pin Socket= 1\*500W

Total= 1160W  
 $P = V * I * 0.9$   
Here,  
 $I = 1160 / 230 * 0.9 = 5.6A$

## Switchboard-6

- Light= 2\*40W
- Fan= 1\*80W
- 2pin Socket= 1\*500W

Total= 660W  
 $P = V * I * 0.9$   
Here,  
 $I = 660 / 230 * 0.9 = 3.2A$

## Switchboard-7

- Light= 1\*40W

Total= 40W  
 $P = V * I * 0.9$   
Here,  
 $I = 40 / 230 * 0.9 = 0.2A$

## Switchboard-8

- Light= 2\*40W
- Fan= 1\*80W
- TV Socket= 1\*500W
- 2pin Socket= 1\*500W

Total= 1160W  
 $P = V * I * 0.9$   
Here,  
 $I = 1160 / 230 * 0.9 = 5.6A$

## Switchboard-9

- Light= 2\*40W
- Fan= 1\*80W
- TV Socket= 1\*500W
- 2pin Socket= 1\*500W

Total= 1160W  
 $P = V * I * 0.9$   
Here,  
 $I = 1160 / 230 * 0.9 = 5.6A$

## Switchboard-10

- Light= 1\*40W

Total= 40W  
 $P = V * I * 0.9$   
Here,  
 $I = 40 / 230 * 0.9 = 0.2A$

## Switchboard-11

- Light= 1\*40W

Total= 40W  
 $P = V * I * 0.9$   
Here,  
 $I = 40 / 230 * 0.9 = 0.2A$

## Switchboard-12

- Light= 1\*40W
- Exhaust Fan= 1\*60W
- 2pin Socket= 1\*500W

Total= 600W  
 $P = V * I * 0.9$   
Here,  
 $I = 600 / 230 * 0.9 = 2.9A$

## Switchboard-13

- Light= 1\*40W
- Chandelier= 1\*60W
- 2pin Socket= 1\*500W

Total= 600W  
 $P = V * I * 0.9$   
Here,  
 $I = 600 / 230 * 0.9 = 2.9A$

## Switchboard-14

- Light= 2\*40W
- Exhaust Fan= 1\*60W
- 2pin Socket= 1\*500W

Total= 640W  
 $P = V * I * 0.9$   
Here,  
 $I = 640 / 230 * 0.9 = 3.1A$

# CIRCUIT BREAKER SELECTION FOR SWITCHBOARD GROUPS

## Group-1

For, Switchboard 1,2,3,4,5,6,7

$I =$

$$(5.6 + 2.9 + 0.09 + 0.09 + 5.6 + 3.2 + 0.2)$$

A

$$= 17.68 \text{ A}$$

So, 20A Circuit Breaker chosen.

## Group-2

For, Switchboard 8

$$I = 5.6 \text{ A}$$

So, 10A Circuit Breaker chosen.

## Group-3

For, Switchboard

9,10,11,12,13,14


$$I = (5.6 + 0.2 + 0.2 + 2.9 + 2.9 + 3.1) \text{ A}$$

$$= 14.9 \text{ A}$$


So, 20A Circuit Breaker chosen.

# SWITCHBOARD GROUPING


## GROUP1

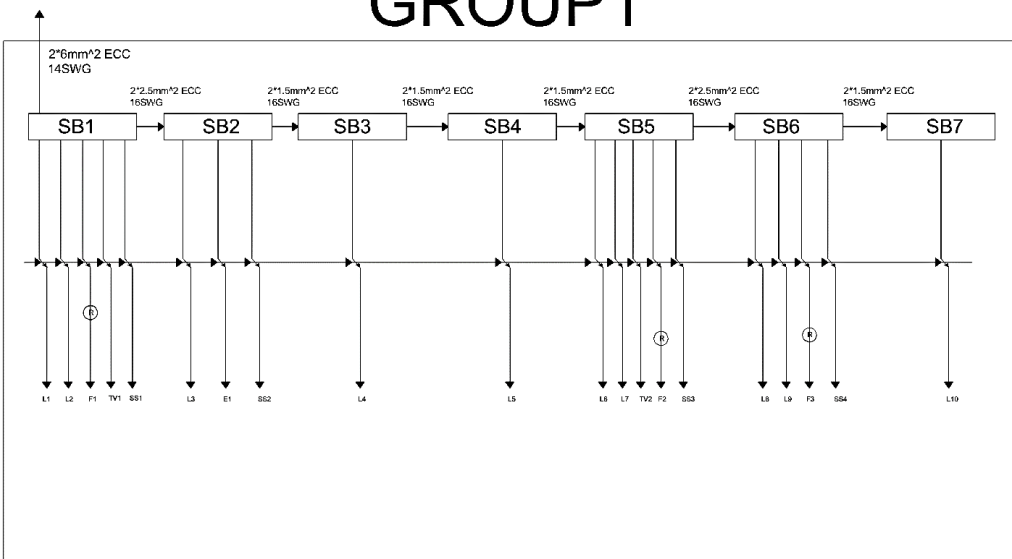

## GROUP2

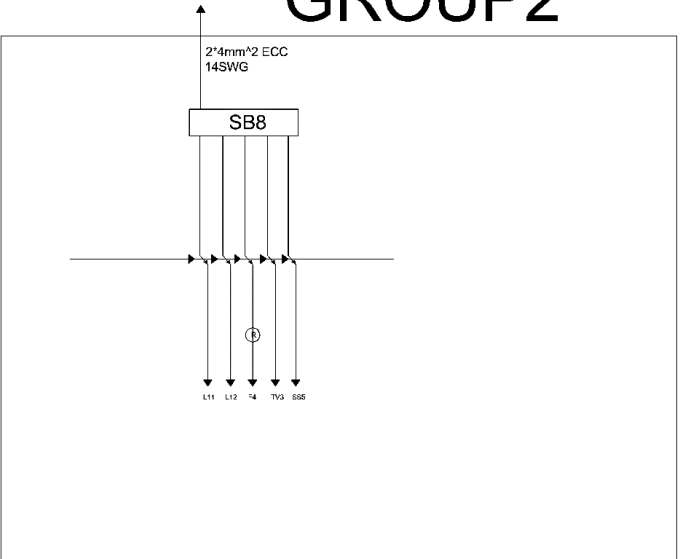

## GROUP3

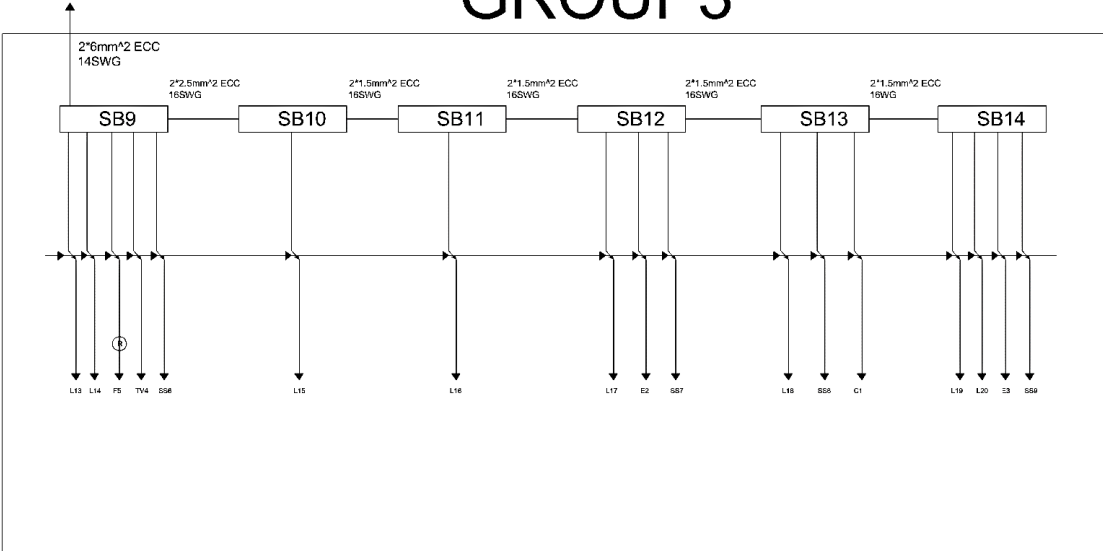

# CALCULATION FOR SDB

## 3-Pin Socket 15A

$$9 \times 3S = (9 \times 1500) \text{ W} \\ = 13500 \text{ W}$$

## AC 20A

$$1 \times M = (1 \times 2500) \text{ W} \\ = 2500 \text{ W}$$

## Total Power

$$= (7896 \times 0.6) + (13500 \times 0.7) + (2500 \times 1) \text{ W} \\ = 16687.6 \text{ W}$$

48 KW > 16.69KW > 9 KW So, required 3 phase line and supply must be 415V L<sub>L</sub>.

$$\text{Now, } P = 1.73 \times V_L \times I_L \times 0.9$$

$$\text{Here, } I_L = 16687.6 / (1.73 \times 415 \times 0.9) \text{ A} \\ = 25.83 \text{ A}$$

$$\text{Including Safety Factor, } I = (I_L \times S.F.) + I_{\text{spare}} \\ = [(25.83 \times 1.5) + 15] \text{ A} \\ = 53.74 \text{ A}$$

So, 60A 440V TP Circuit Breaker chosen.

# CALCULATION FOR MDB

$$\text{Every Unit} = 16687.6 \text{ W}$$

$$10 \text{ Units} = 10 \times 16687.6 \text{ W} \\ = 166.876 \text{ KW}$$

## Extra Load (Lights at lift and staircase),

$$\text{Number of load} \times \text{Load value} \times \text{Number of floor} \\ = 4 \times 40 \times 5 \text{ W} \\ = 800 \text{ W}$$

## Water Pump (1 of 7HP),

$$= 7 \times 746 \text{ W} \\ = 5222 \text{ W}$$

## Lift (Single lift),

Chosen 800Kg lift (Around 8 person)

$$\text{Speed} = 1.8 \text{ m/s}$$

$$\text{Motor Capacity} = 9 \text{ KW}$$

$$\text{MCCB Capacity} = 30 \text{ A}$$


$$\text{Total Power} = (166.876 + 0.8 + 5.222 + 9) \text{ KW} \\ = 181.9 \text{ KW}$$

$$\text{Now, } P = 1.73 \times V_L \times I_L \times 0.9$$


$$\text{Here, } I_L = (181.9 \times 1000) / (1.73 \times 415 \times 0.9) \text{ A} \\ = 281.52 \text{ A}$$

So, 300A TP Circuit Breaker chosen.



# SUB-DISTRIBUTION BOARD DIAGRAM

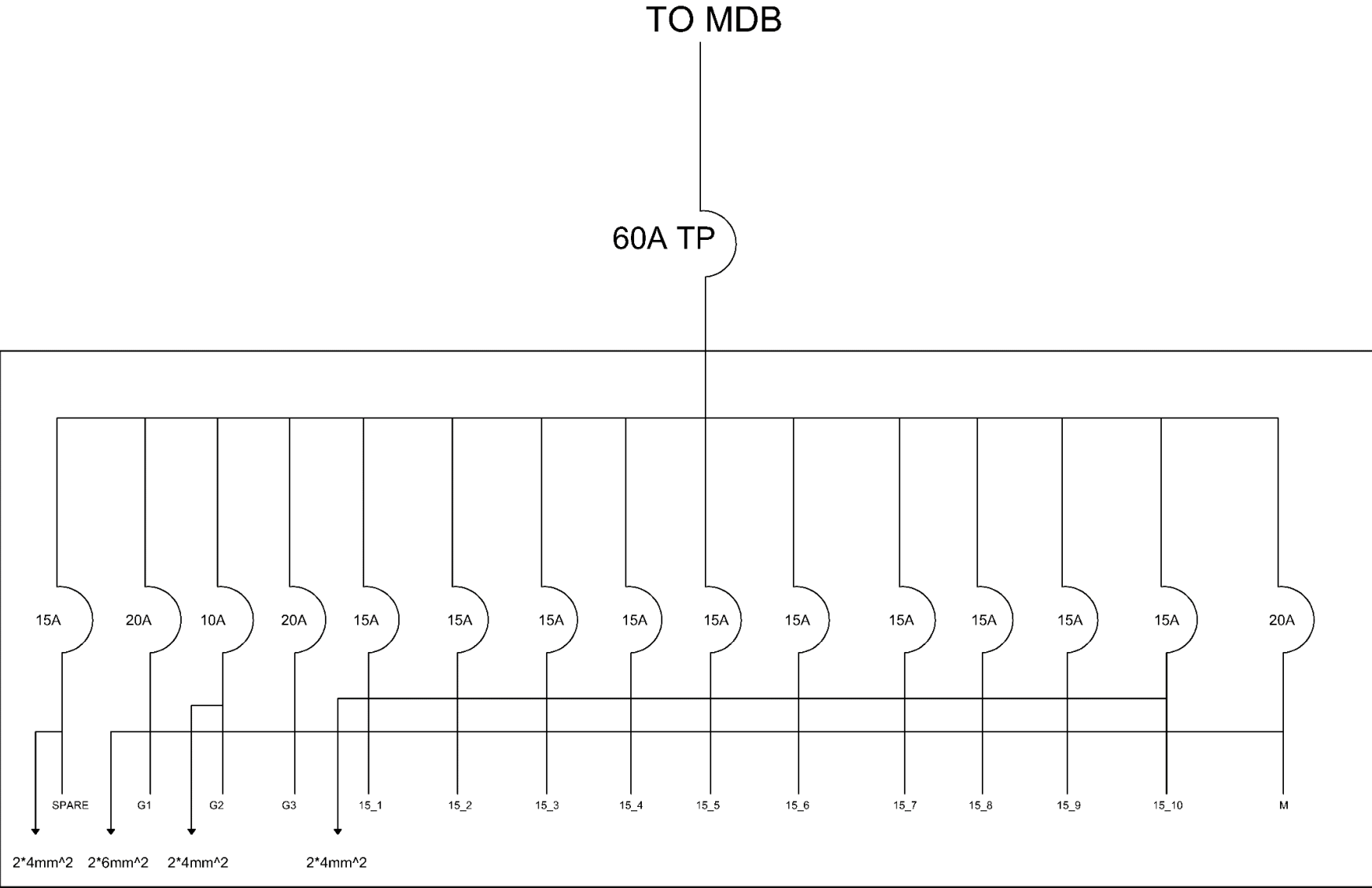

# MAIN DISTRIBUTION BOARD DIAGRAM

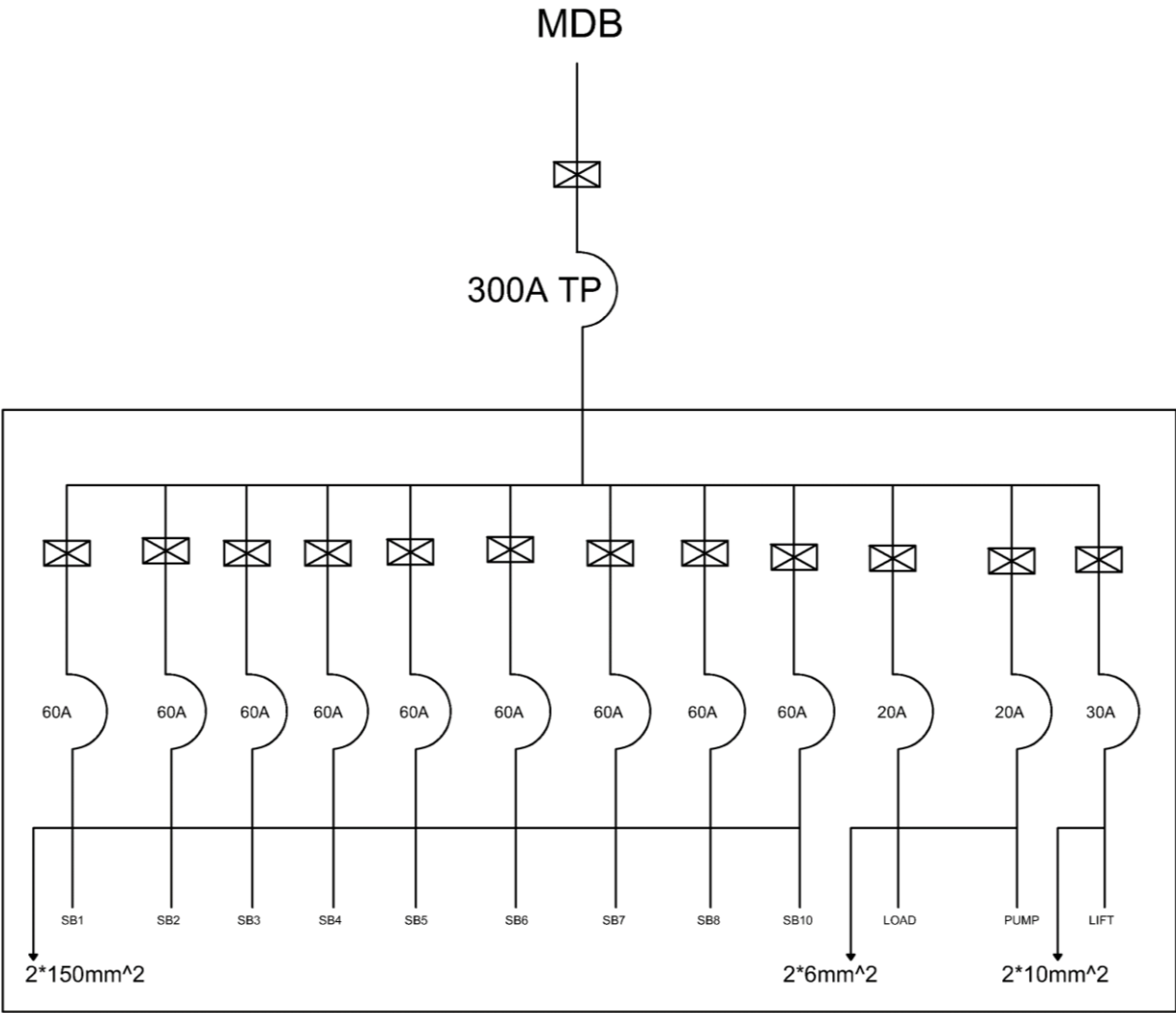
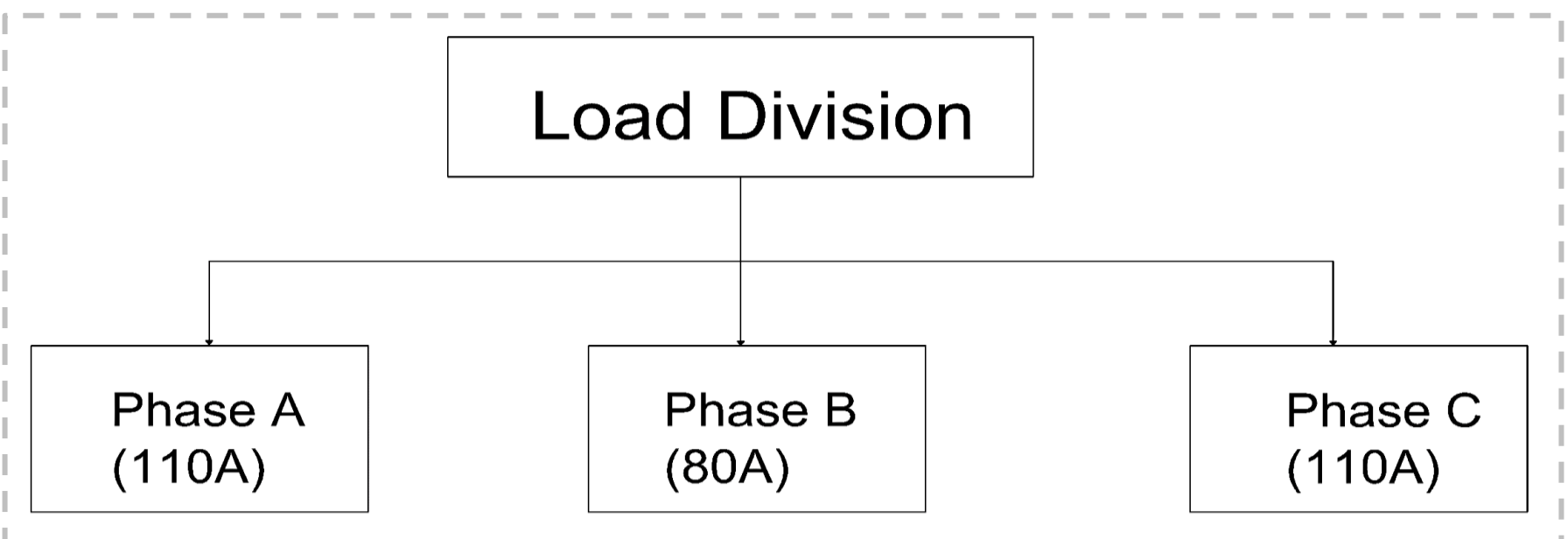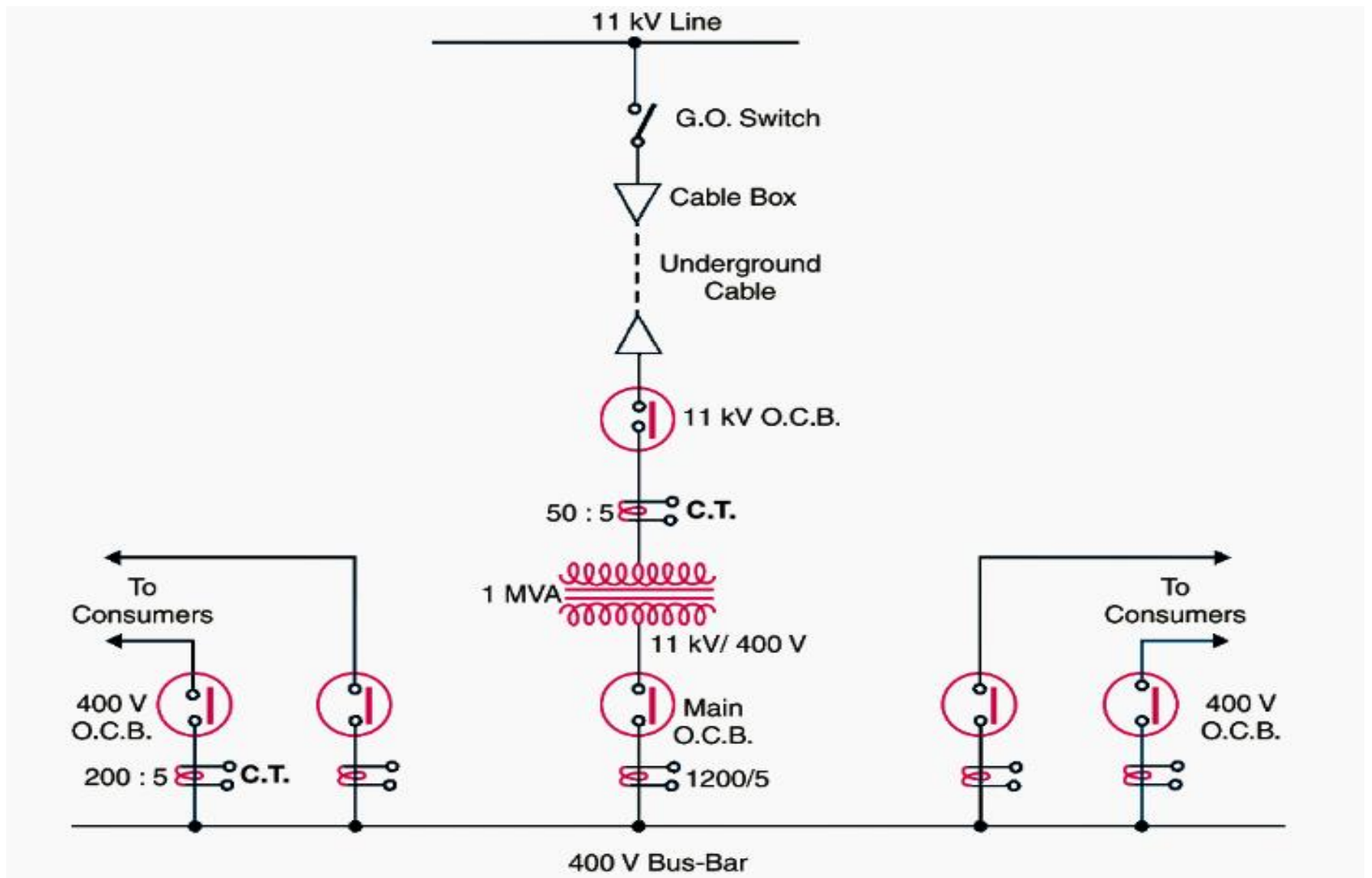
# SINGLE LINE DIAGRAM OF A TYPICAL 11KV/400V INDOOR SUBSTATION 11KV LINE



# PV CALCULATION

Rooms	Light[T1]	Light[L]	Chandelier	Fan	TV
Bed	0	6	0	3	1
Toilet	2	2	0	0	0
Closet	2	0	0	0	0
Balcony	0	3	0	0	0
Kitchen	0	2	0	0	0
Drawing	0	2	0	1	1
Dinning	0	3	1	1	0

Content	Number	Power[Watt]	Usage[hr]	Energy[Whr]
Light[T1]	4	18	9	648
Light[L]	18	40	9	6480
Chandelier	1	60	6	360
Fan	5	80	9	3600
TV	2	500	6	6000

[ **Total energy consumption** = 17088 Whr [*Each unit*]

[Note. 5 storied building, each floor 2 units.]

For, Each floor =  $(17088 \times 2)$  Whr = 34176Whr

For, All floors [**10 units**] =  $(34176 \times 5)$  Whr = 170880Whr

Now, **Total energy consumption** for entire building at 5% load,

$$E = 170880 \times 0.05 = 8544 \text{Whr}$$

Here, **Total power consumption** each floor =  $(2252 \times 2)$  W = 4504W

Now, **Total power consumption** for entire building at 5% load,

$$P_{\text{total}} = (4504 \times 5) \times 0.05 \text{ W} = 1.126 \text{KW} \text{ [Here, system nominal voltage 12V]}$$

[Note. If system processing up to about 1.5KW- hr then system nominal voltage is 12 volts]

**Total energy & power consumption**

## **[ Chosen Solar Panel Model - STM435/120-S3**

Maximum Power = 435W

Maximum Voltage ( $V_{mp}$ ) = 33.76V

Maximum Current  $I_{MAX-PV}$  = 12.89A

Open Circuit Voltage  $V_{OC}$  = 40.8V

Nominal Output Voltage = 12V

Short Circuit Current  $I_{SC}$  = 13.34A **] Solar panel Model**

**[ Total Amp-hr per Day** = Total System Load/(Inverter loss\*System Nominal Voltage)

$$= 8544/(0.85*12) \text{ Amp-hr/day} = 837.65 \text{ Amp-hr/day}$$

**Total Amp-hr per Day with Batteries** = Total Amp-hrs/Day\*Losses and safety factor

$$= 837.65 \text{ Amp-hr/day} * 1.25$$

$$= 1047.063 \text{ Amp-hr/day} **] Battery side calculation**$$

**[ Now, Parallel PV Module**

= Total energy in Whr/(T peak solar\*nPV\*nINV\*nBATTERY\*VS.Nominal\*Imax-PV)

$$= 8544/(7*0.9*0.85*0.8*12*12.89) = 12.89 = 14 \text{ Module}$$

Now, **Series PV Module**

=  $V_{sys} \text{ Nominal} / V_{pv} \text{ Nominal}$

$$= 12/12 = 1 \text{ Module}$$

**Total No. of PV Module** = No. of parallel PV module/ No. of series PV module

$$= 14*1 = 14 \text{ Module} **] No. PV calculation**$$



**[ Chosen Lithium Battery Model - RB300 12V 300Ah LiFePO4 Battery.**

Voltage = 12V

Amp hours = 300Ah

Desired Reserve Time (Days) = 2 days

**Now Minimum Battery Capacity**

$$\begin{aligned}\text{Battery Hours} &= (\text{Total Amp-hr per day} * \text{Desired Reserve Time}) / 0.80 \\ &= (1047.063 * 2) / 0.80 = 2617.66 \text{Amp-hr}\end{aligned}$$

**Number of Batteries in Parallel**

$$\begin{aligned}\text{Parallel Batteries} &= \text{Required Battery Capacity} / \text{Capacity of Selected Battery} \\ &= 2617.66 / 300 = 8.72 = 8 \text{ Batteries}\end{aligned}$$

**Number of Batteries in Series**

$$\begin{aligned}\text{Series Batteries} &= V_{\text{sys Nominal}} / V_{\text{battery}} \\ &= 12 / 12 = 1 \text{ Battery}\end{aligned}$$

**Total No. of Batteries** = No. of parallel batteries \* No. of series batteries

$$= 8 * 1 = 8 \text{ Batteries} ] \text{ No. Battery calculation}$$

**[ Charge Controller Size = (PVparallel \* IPV<sub>sc</sub> \* S.F.) Amp**

$$= (14 * 13.34 * 1.25) \text{ Amp}$$



$$= 233.45 \text{Amp} ]$$

**[ Inverter Size = (Ptotal \* S.F.)**

$$= (1.126 * 1.25)$$


$$= 1.41 \text{KW} ]$$

# PV DIAGRAM

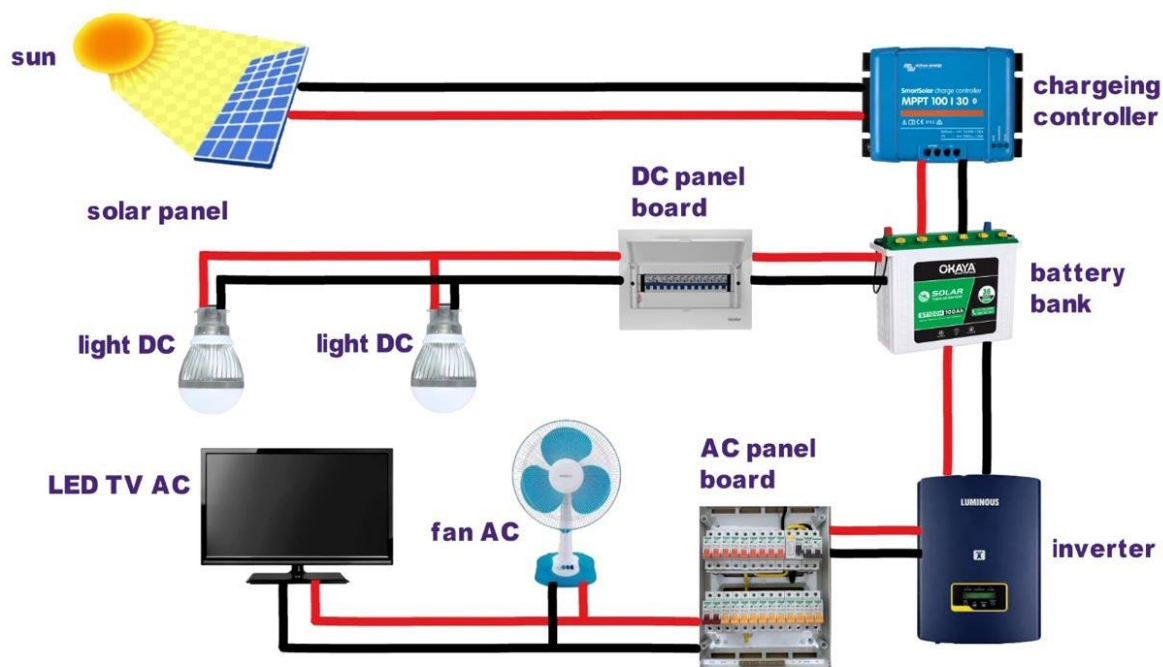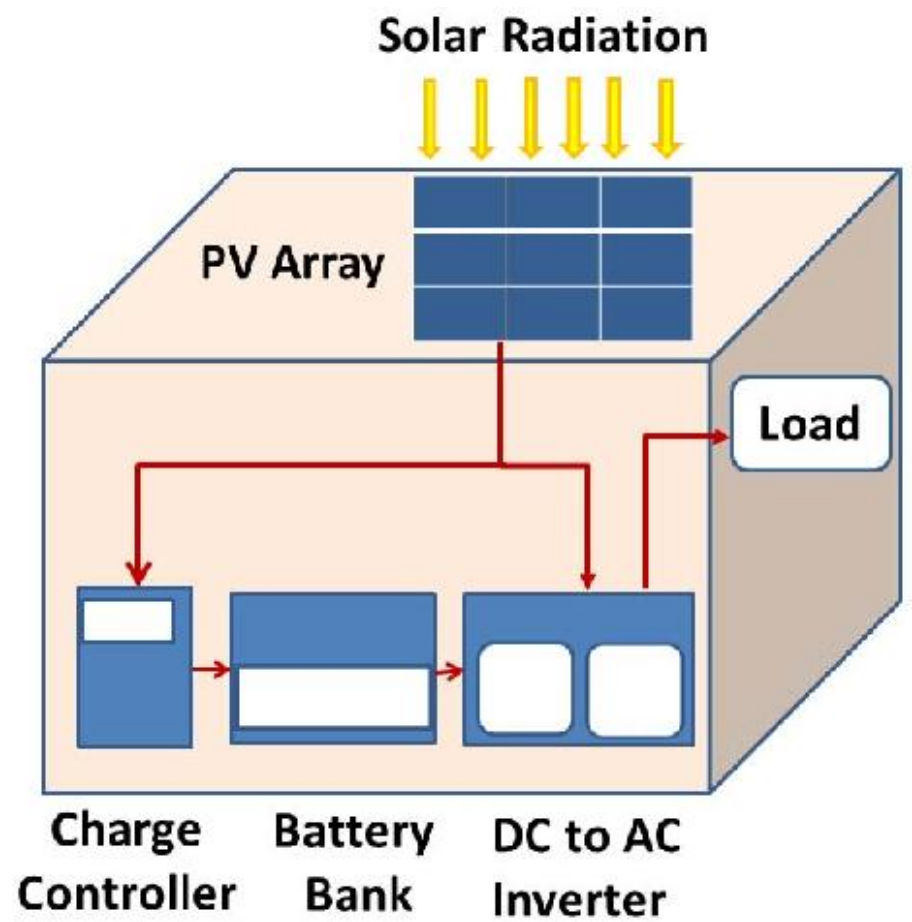



# EARTHING SYSTEM
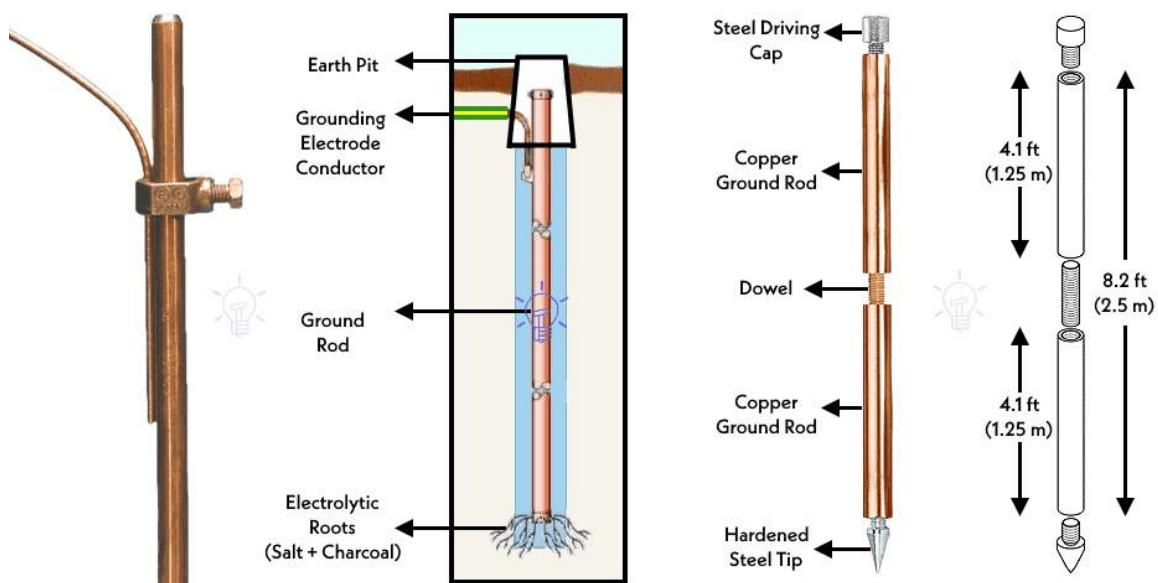
## Ground Rod in the Grounding System - Sizing & Installation



# EMERGENCY FIRE PROTECTION SYSTEM

## ADDRESSABLE FIRE ALARM SYSTEM

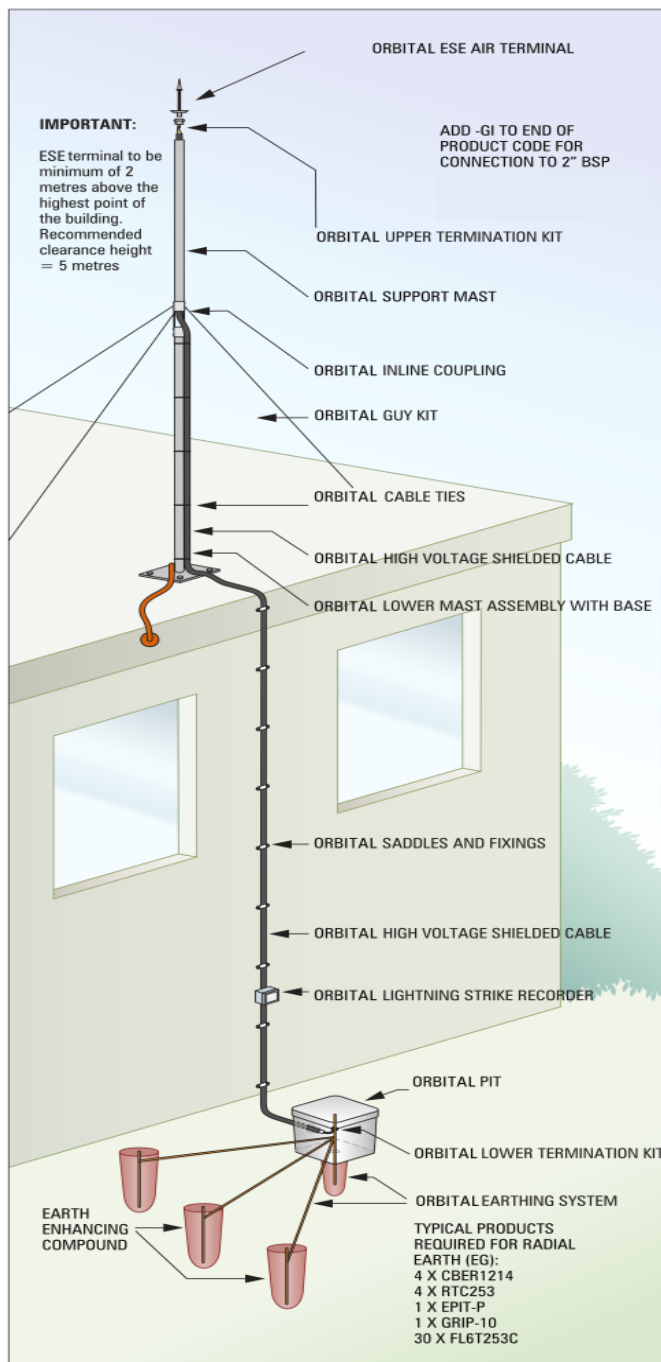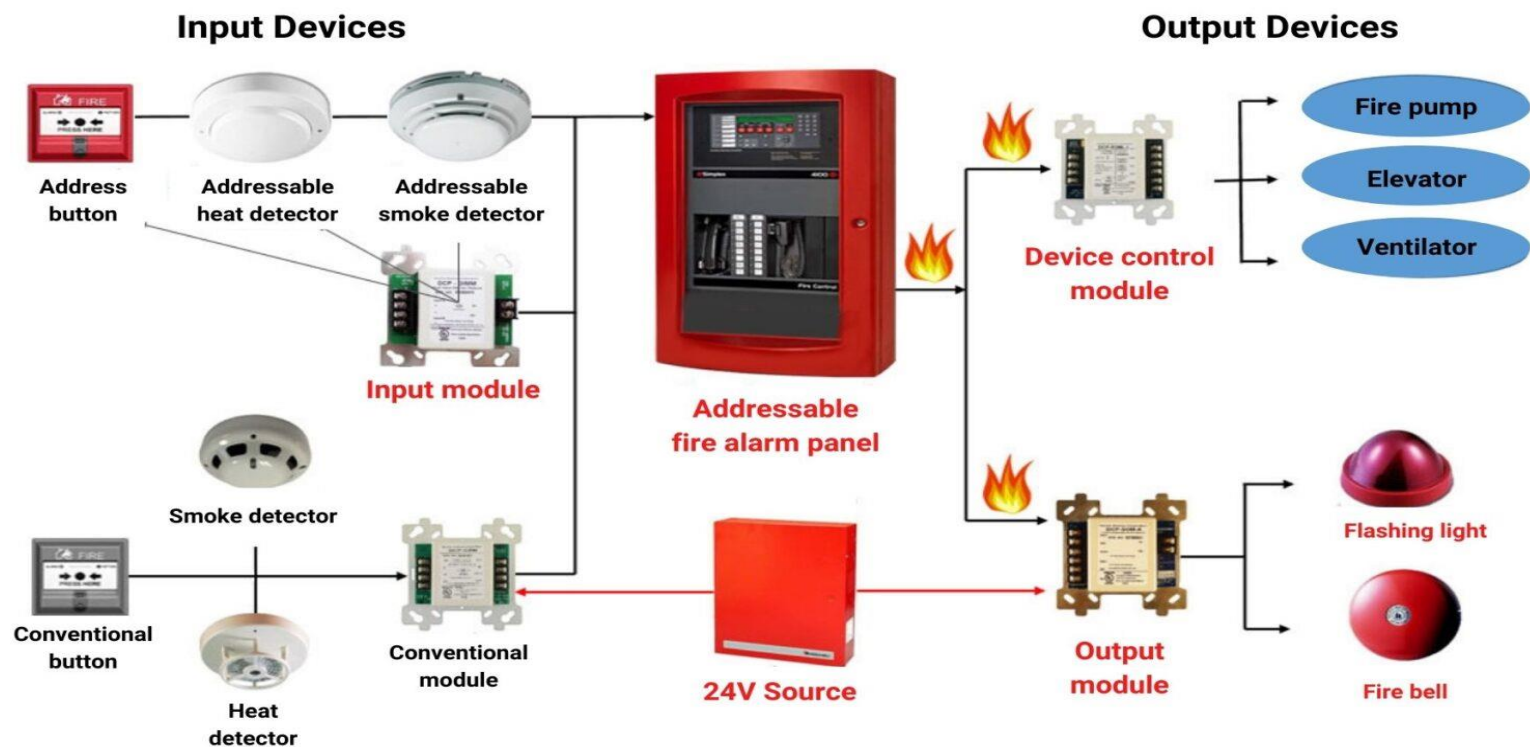

## LIGHTENING PROTECTIONSYSTEM

THANK YOU